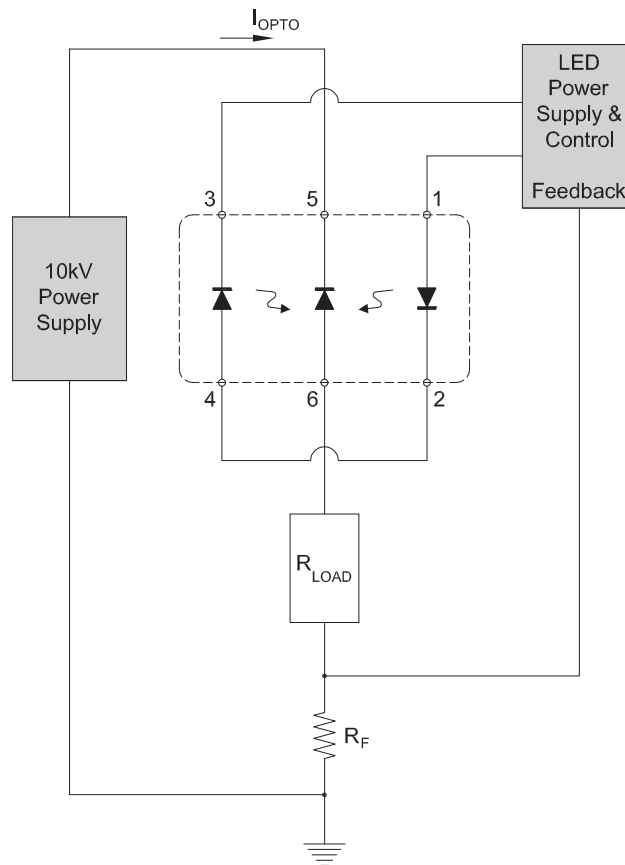




# Optocoupler Application Note

## Example of a High Voltage Linear Regulator Circuit



### Circuit Notes / Application Considerations

- Gain of optocoupler dependent on applied voltage and individual device characteristics.
- Output voltage can be determined with the following formula:  
$$V_{LOAD} = (I_{OPTO}) * (R_{LOAD})$$
$$= (I_{LED} * Gain) * (R_{LOAD})$$

For  $R_F \ll R_{LOAD}$
- A resistor can be placed in series with the load and high voltage diode to limit the current through the HV diode and to the load.
- The LED feedback circuit is necessary to account for changes in the gain of the device that can arise from applied voltage to the HV diode, changes in device temperature, and LED aging.

Dimensions: In. (mm) • All temperatures are ambient unless otherwise noted. • Data subject to change without notice.



**Voltage Multipliers Inc.**

8711 W. Roosevelt Ave.  
Visalia, CA 93291 USA

Tel: 559.651.1402  
Fax: 559.651.0740

[www.voltagemultipliers.com](http://www.voltagemultipliers.com)  
[www.highvoltagepowersupplies.com](http://www.highvoltagepowersupplies.com)